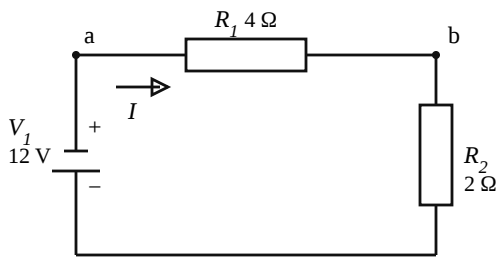



Circuits practice

Write your KVL and KCL equations under each circuit, then the values asked for. Use the names printed on the diagram.


1. Write KVL around the loop and find the current I .



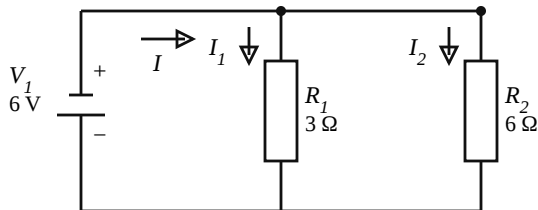2. Write KCL at the top node and find I_1 , I_2 and the source current I .



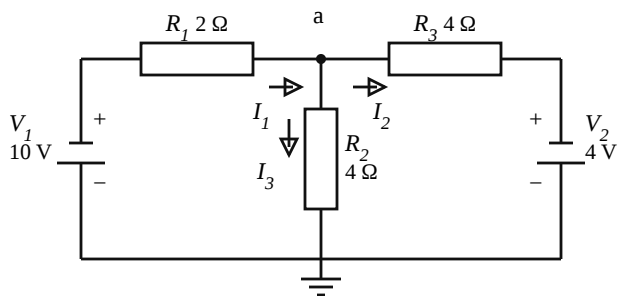3. Find V_a , then I_1 , I_2 and I_3 . Write KCL at node a, or KVL around each loop.



4. Find V_a and V_b by writing KCL at nodes a and b.

